

Voltage Drop in final and distribution circuits.


The following questions concern voltage drop in consumers' installations.

Reference: BS7671:2008 +A1 2011, Appendix 4, Section 6.4

Question 1: Complete the following table by expressing the maximum voltage drop as a percentage (%)

| Supply arrangement | Lighting | Other |
|--|----------|-------|
| Low voltage installations supplied directly from a public low voltage distribution system | 3% | 5% |
| Low voltage installation supplied from private low voltage supply. Note: voltage drop in each final circuit should not exceed the values given for low voltage public distribution systems | 6% | 8% |

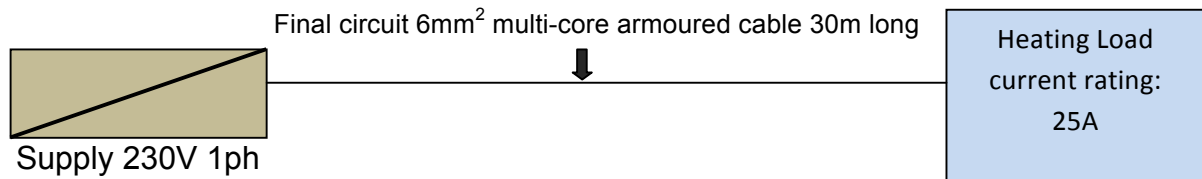Example 1: Calculate the voltage drop for the following arrangement



The actual voltage drop (AVD) can be determined from the formula:

$$\text{AVD} = \frac{\text{mV/A/m} \times \text{Ib} \times \text{Length of cable run}}{1000}$$

From cable table 4D4B the mV/A/m for the cable is 7.3 then the voltage drop can be determined

$$\text{AVD} = \frac{7.3 \times 25 \times 30}{1000} = \mathbf{5.48 \text{ Volts}}$$

Check that the voltage drop does not exceed the allowance of 5% nominal voltage:

$$\text{Voltage drop allowed} = \% \times 230$$


$$\text{Voltage drop allowed} = \frac{5}{100} \times 230 = \mathbf{11.5 \text{ Volts}}$$

Conclusion: The cable is suitable.

Try these problems:

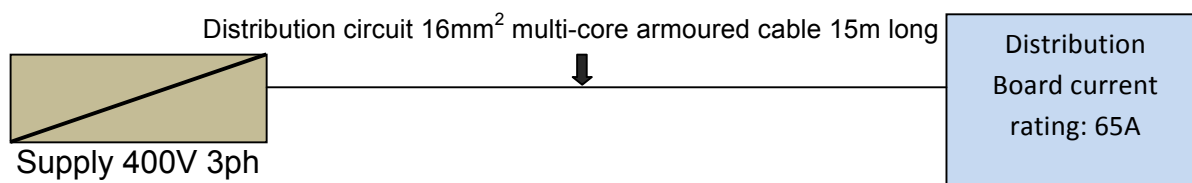Question 2:

Calculate the voltage drop for the following arrangement



$$\text{AVD} = \frac{\text{mV/A/m} \times \text{Ib} \times \text{Length of cable run}}{1000}$$

From Table 4D4B the mV/A/m for the cable is 2.4, therefore the AVD is:-

$$\text{AVD} = \frac{2.4 \times 65 \times 15}{1000} = \mathbf{2.34 \text{ Volts}}$$


$$\text{Voltage drop allowed} = \% \times 400$$

$$\text{Voltage drop allowed} = \frac{5}{100} \times 400 = \mathbf{20 \text{ Volts}}$$

Conclusion: The cable is suitable.

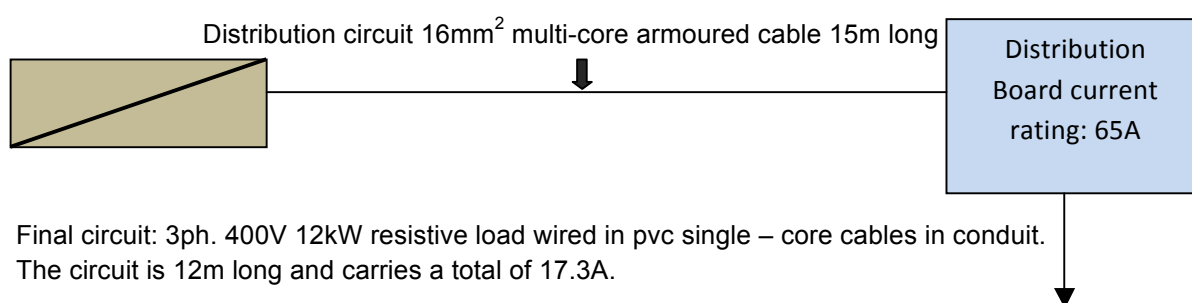Question 3:

Calculate the voltage drop of a final circuit originating at the distribution board in question 2 above if the circuit details are as follows:



Final circuit: 3ph. 400V 12kW resistive load wired in pvc single – core cables in conduit. The circuit is 12m long and carries a total of 17.3A.

$$\text{AVD} = \frac{\text{mV/A/m} \times \text{Ib} \times \text{Length of cable run}}{1000}$$

From Table 4D1B the mV/A/m for the cable is 15, therefore the AVD is:-

$$\text{AVD} = \frac{15 \times 17.3 \times 12}{1000} = \mathbf{3.14 \text{ Volts}}$$

Conclusion: The cable is suitable.

Note:

The voltage drop between the origin of an installation and the load - end of a final circuit should not be greater than the percentages stated in Table 4Ab of BS7671. In the case of questions 2 and 3 above, the voltage drop for the distribution circuit should be added to the voltage drop of the final circuit to ensure the percentage allowed, (5% of nominal voltage), is not exceeded.

Voltage drop from origin to load of final circuit is:

2.34V (Distribution circuit) + 3.14V (final circuit) = **5.48V** (this is fine)